

The logo for the International Physics Olympiad 2016. It features a large, tilted oval shape. The outer border of the oval is a thick blue line. Inside this is a thick green ring. The center of the oval is white. In the center of the white area, the text 'IPhO 2016' is written in a large, bold, black sans-serif font. Below this text is a solid black circle. To the left of the black circle, the text 'International Physics Olympiad Switzerland Liechtenstein' is written in a smaller, bold, black sans-serif font, arranged in four lines.

IPhO 2016



**International
Physics Olympiad
Switzerland
Liechtenstein**

T2: Nonlinear Dynamics in Electric Circuits


10 points

Anton Alekseev


Yves Barmaz

Pavel Rodin


Motivation

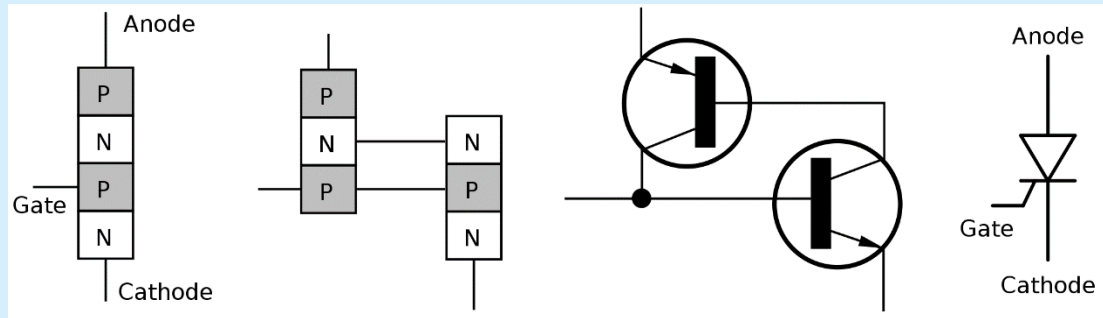

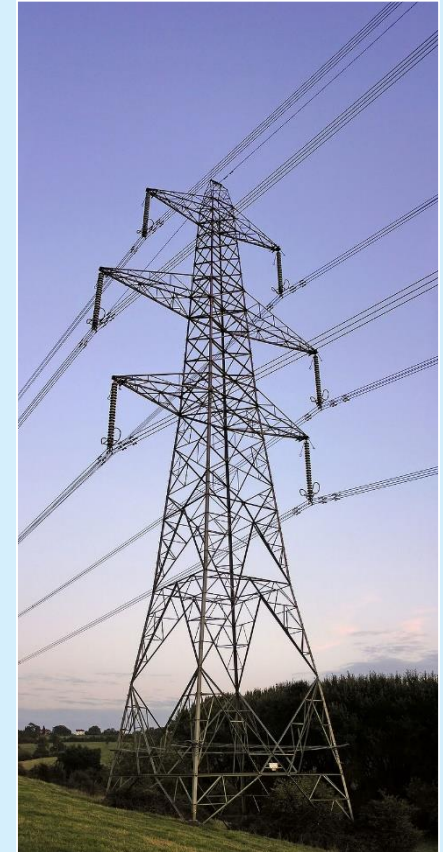
Bi-stable elements (e.g. thyristors) are used in controlling currents in high voltage power lines.



Motivation

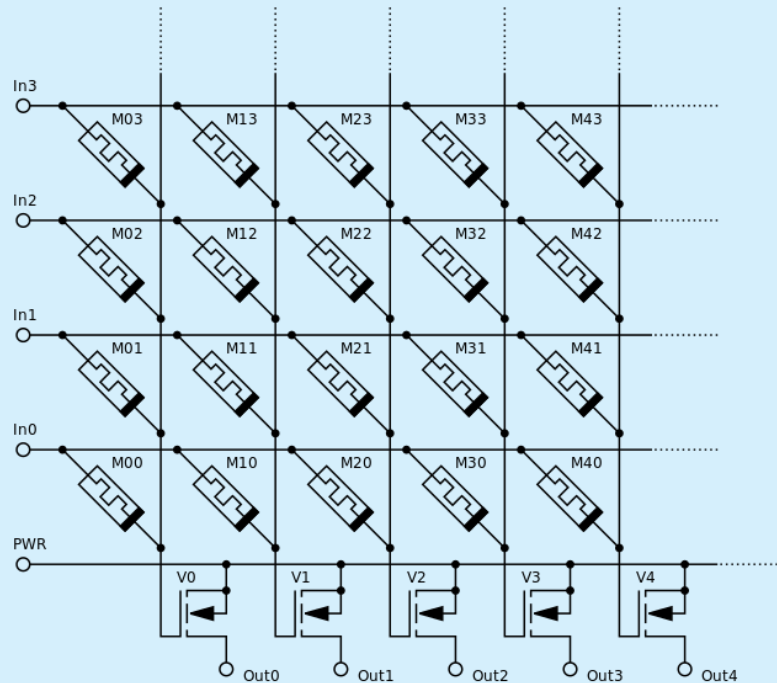

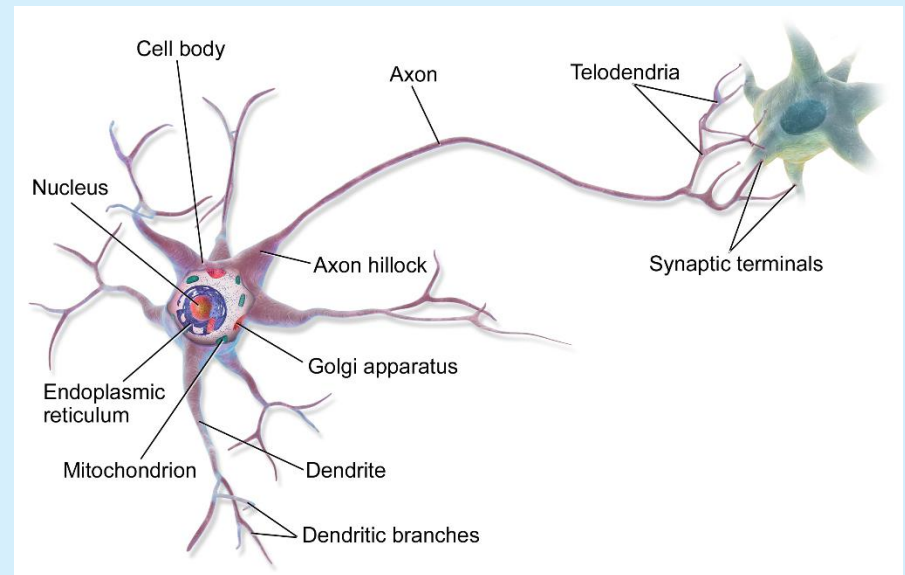
Bi-stable elements are used to model the behavior of neurons and neuron networks in the brain.



Objectives

- To study stability and instability of stationary states of a bi-stable element;
- To discover non-linear oscillations in a circuit with a bi-stable element
- To study a simple model of a neuristor


Theoretical background

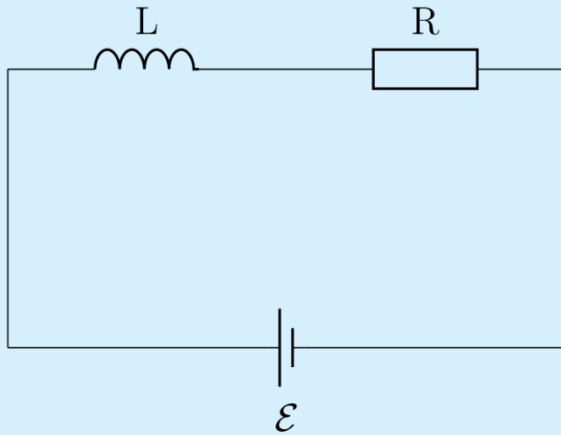

- Dynamics of RL -circuit

$$RI + L \frac{dI}{dt} = \mathcal{E}$$
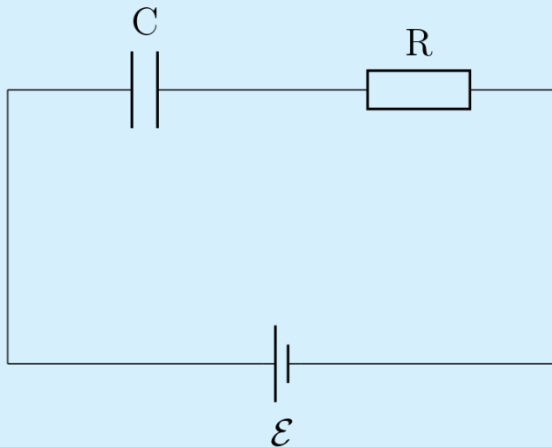
$$I(t) = \frac{\mathcal{E}}{R} + \left(I(0) - \frac{\mathcal{E}}{R} \right) e^{-\frac{R}{L}t}$$




- Dynamics of RC -circuit

$$\frac{Q}{C} + R \frac{dQ}{dt} = \mathcal{E}$$

$$Q(t) = C\mathcal{E} + (Q(0) - C\mathcal{E})e^{-\frac{t}{RC}}$$


Theoretical background

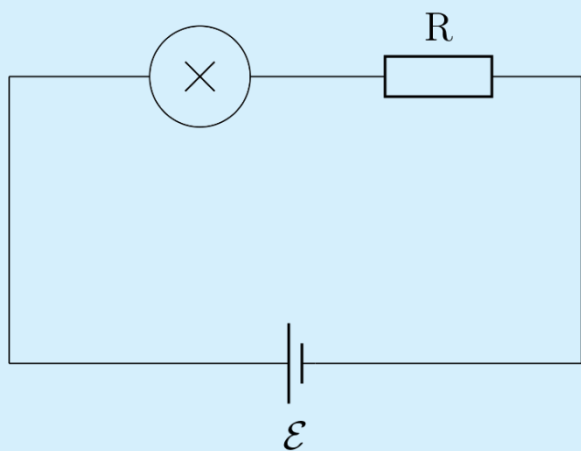


$$U_X + I_X R = \mathcal{E}$$

$$I_X = \frac{\mathcal{E} - U_X}{R}$$

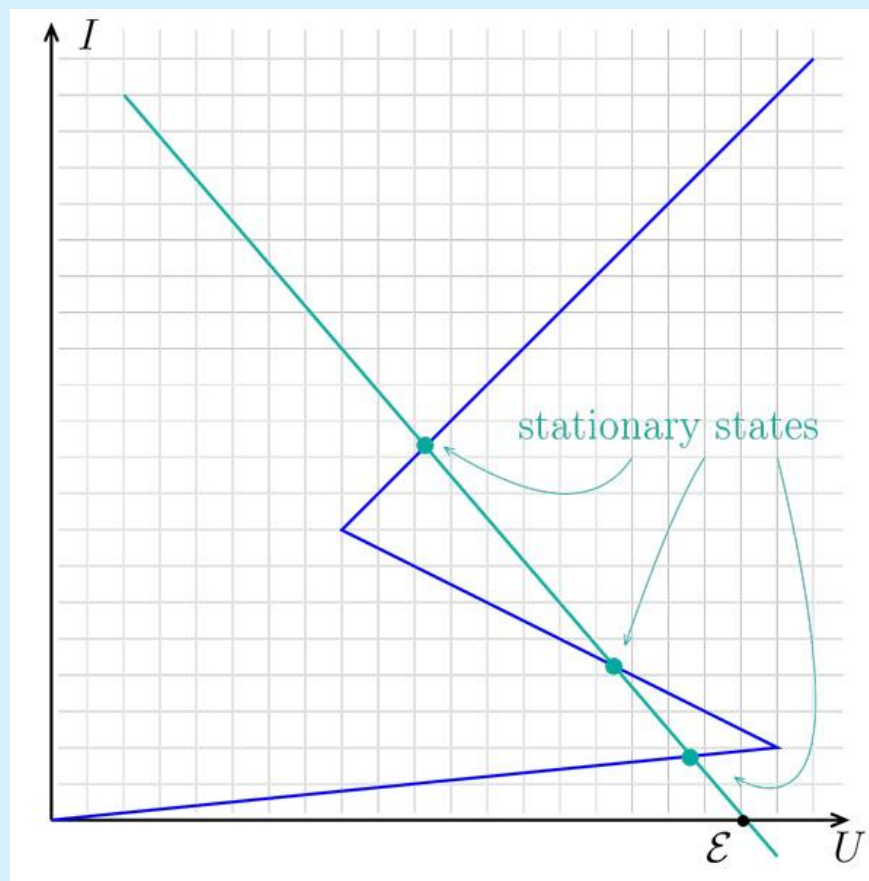stationary states are intersections of this line with the I-V graph



Task A (3 points)

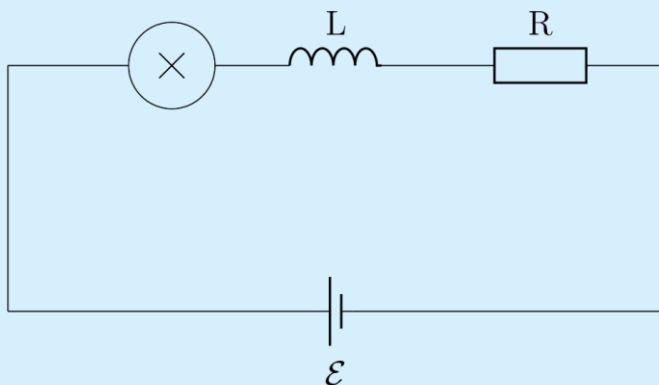

- Study of stability of a circuit with a non-linear element

$$U_X + L \frac{dI_X}{dt} + RI_X = \mathcal{E}$$

- Stationary state on the middle branch

$$U_X = R_{int}(I_0 - I_X)$$



$$\Rightarrow L \frac{dI_X}{dt} = (\mathcal{E} - R_{int}I_0) + (R_{int} - R)I_X$$

$$R_{int} - R < 0 \Rightarrow \text{stable}$$

$$R_{int} - R > 0 \Rightarrow \text{unstable}$$

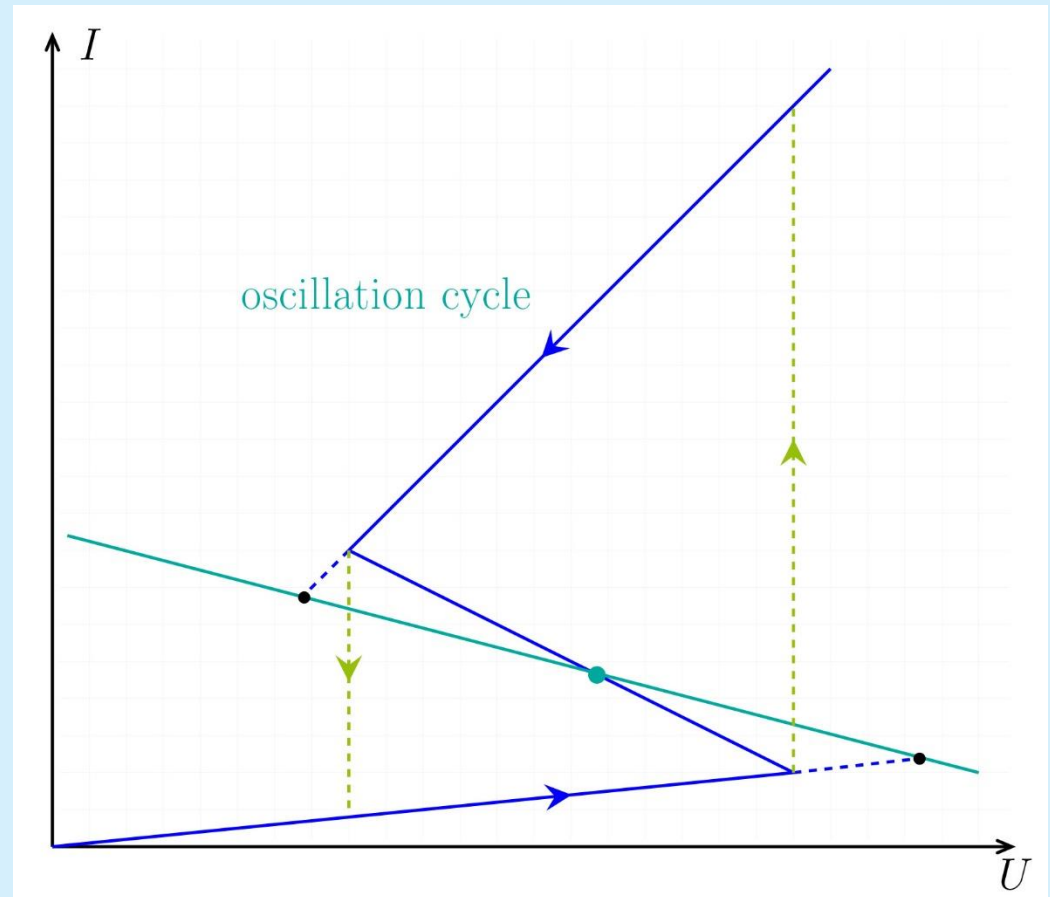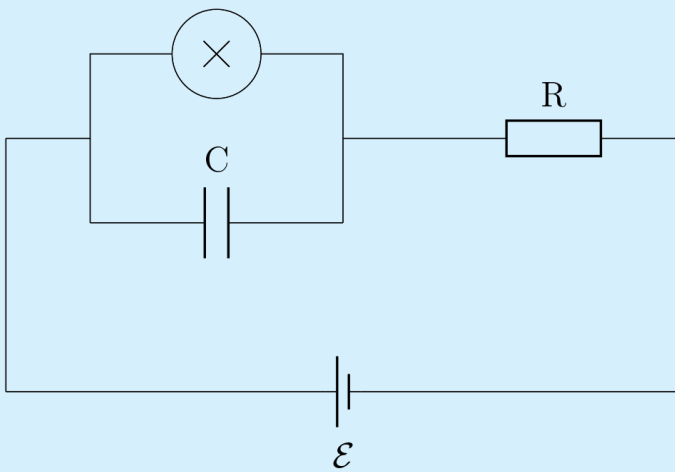
Task B (5 points)

- Study of non-linear oscillations in a circuit with a bi-stable element




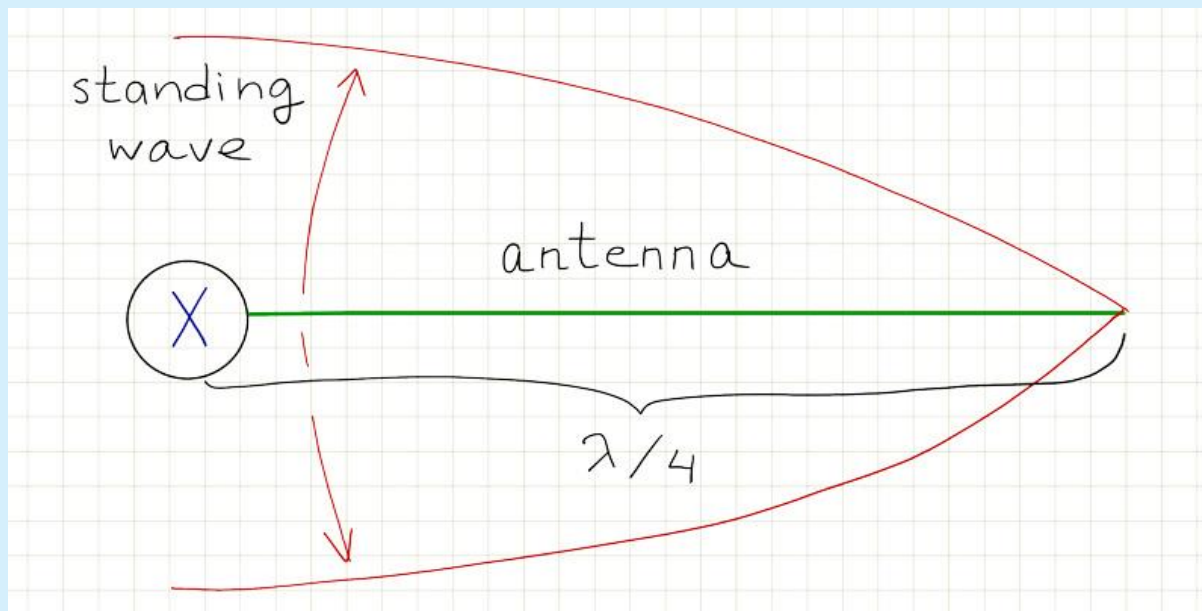Task B (5 points)


- Compute oscillation period
- Estimate power dissipated by the element X
- Build a radio transmitter



Task C (2 points)


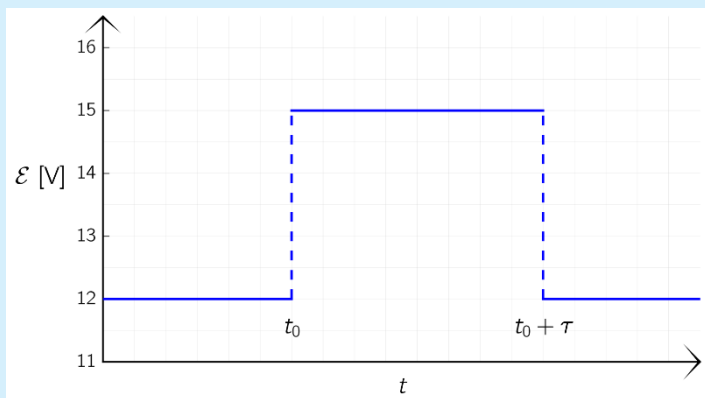


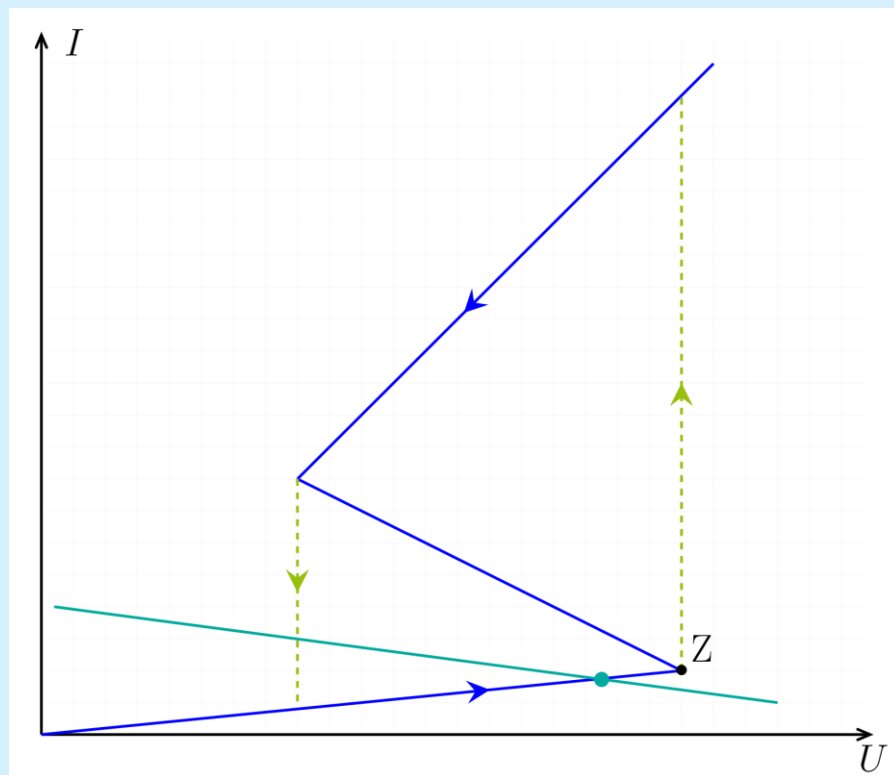- If the system reaches Z $\Rightarrow$ one oscillation $\Rightarrow$ it's a neuristor
- If the system doesn't reach Z $\Rightarrow$ returns to stationary state



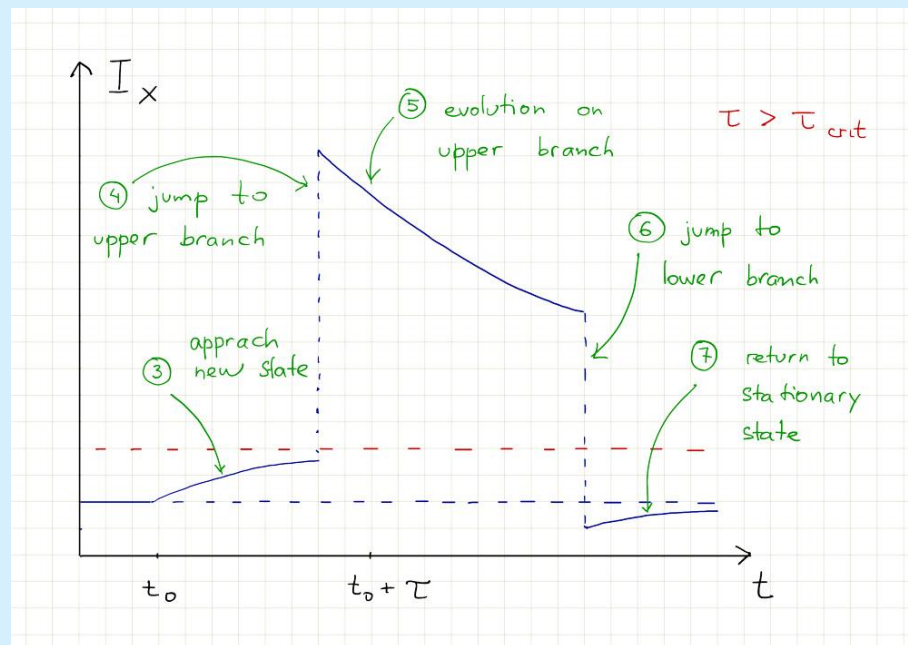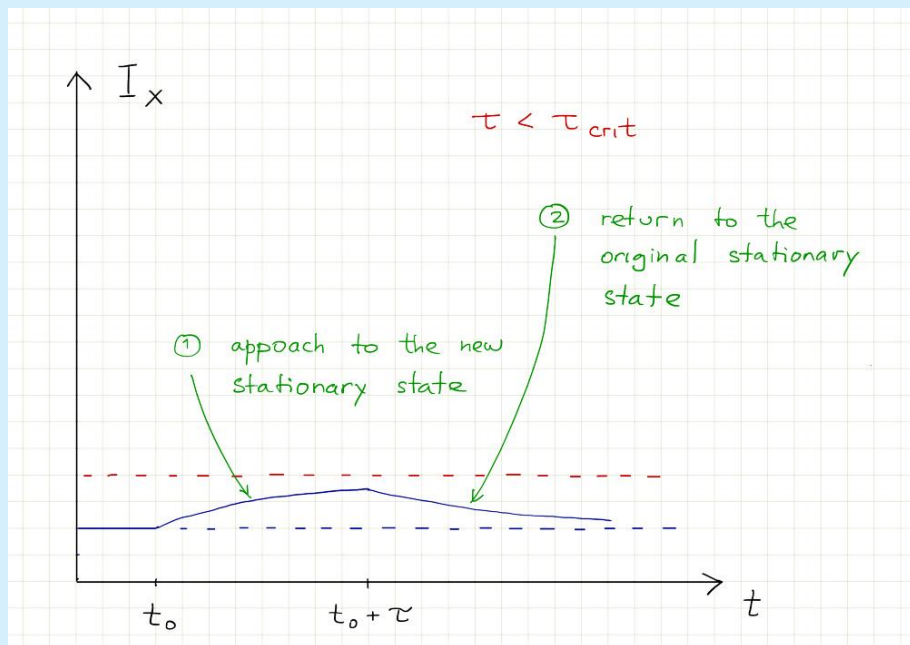Task C (2 points)

The time dependence of the voltage $U_X(t)$ for $\tau < \tau_{crit}$ and for $\tau > \tau_{crit}$



Summary

Part A (3 points)

- Stationary states
- Stability

Part B (5 points)

- Non-linear oscillations
- Power estimate
- Radio transmitter

Part C (2 points)

- Neuristor

What the students are being tested for

Knowledge

2.3.1 Kirchoff's current and voltage laws

2.3.4 Ohm's law, Jule's law, nonlinear elements of given V-I characteristic, time constants of RL and RC circuits

2.4.1 Positive feedback as a source of instability

2.4.3 Wave length

2.4.4 Standing waves

Skills

4.2 Solving simple equations involving logarithmic and exponential functions

4.7 Calculus

4.8 Approximation

Modularity

